

Digital Logic Design + Computer Architecture

Sayandeep Saha

Assistant Professor
Department of Computer
Science and Engineering
Indian Institute of Technology
Bombay




Sequential Circuits

A Circuit that Remembers


- How do you remember things?
 - Memory
- Can we design a circuit which remembers?
 - A formal way to model this capability is called a **state**
 - So we will be modelling circuits to create a **state**.

Remember

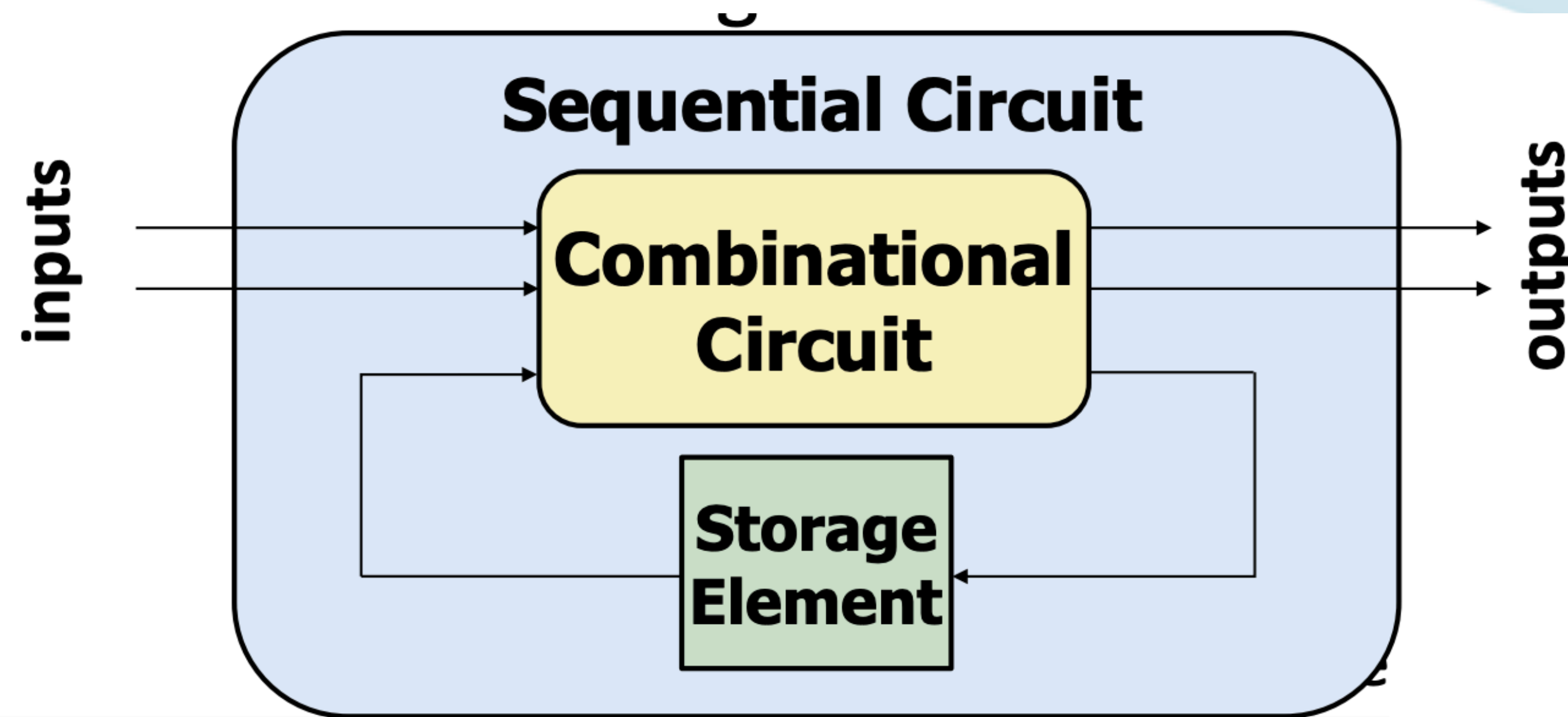


A Circuit that Remembers

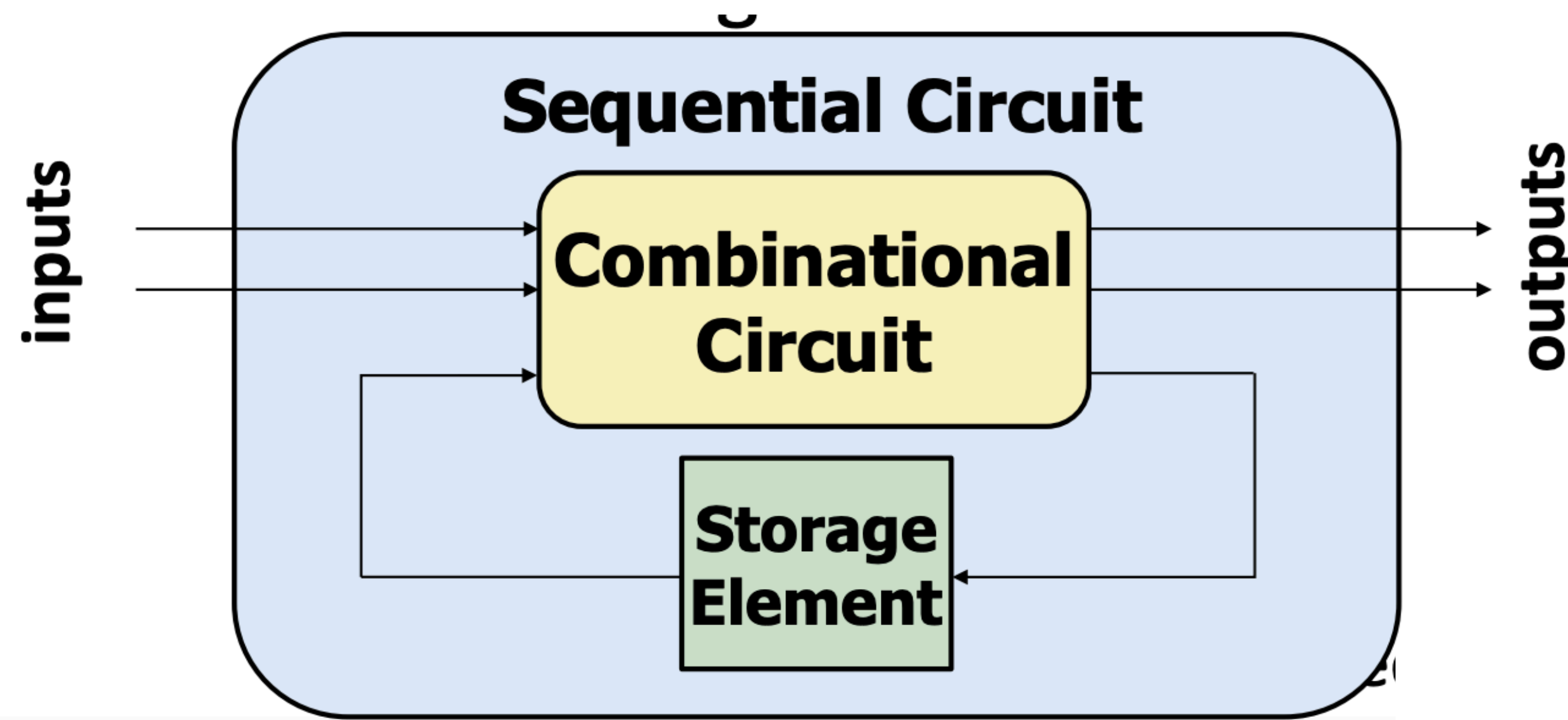- **Every digital logic you see in real life is sequential**
 - Your processors — that you going to see in the rest of the course
 - Your washing machine — it remembers your setting and washes accordingly
 - Your elevator — it remembers which floors to stop
 - Your ATM machine — it remembers your choice and updates your account after despatching money



Sequential Circuits

 


Sequential Circuits

To generate the Y 's: memory devices must be supplied with appropriate input values

- **Characteristic table/functions:** switching functions that describe the impact of x_i 's and y_j 's on the memory-element input
- **Excitation table:** its entries are the values of the memory-element inputs

Most widely used memory elements: **flip-flops**, which are made of **latches**

 - **Latch:** remains in one state indefinitely until an input signals directs it to do otherwise




Memory Element: Latches

Latch: remains in one state indefinitely until an input signals directs it to do otherwise


Set-reset of *SR* latch:



(a) Block diagram.

 

(b) NOR latch.

 

(c) NAND latch.

Memory Element: Latches

Characteristic table and excitation requirements:

$y(t)$	$S(t)$	$R(t)$	$y(t + 1)$
0	0	0	0
0	0	1	0
0	1	1	?
0	1	0	1
1	1	0	1
1	1	1	?
1	0	1	0
1	0	0	1


$$RS = 0$$

$$y(t + 1) = R'y(t) + S$$


<i>Circuit change</i>		<i>Required value</i>	
<i>From:</i>	<i>To:</i>	S	R
0	0	0	—
0	1	1	0
1	0	0	1
1	1	—	0

Clocked SR latch: all state changes synchronized to clock pulses

 - Restrictions placed on the length and frequency of clock pulses: so that the circuit changes state no more than once for each clock pulse



(a) Block diagram.

 

(b) Logic diagram.

Memory Element: Latches

Why is the (1,1) input forbidden?


$y(t)$	$S(t)$	$R(t)$	$y(t + 1)$
0	0	0	0
0	0	1	0
0	1	1	?
0	1	0	1
1	1	0	1
1	1	1	?
1	0	1	0
1	0	0	1

$$RS = 0$$

$$y(t + 1) = R'y(t) + S$$

1. If $R=S=1$, Q and Q' will both settle to 1, which **breaks** our invariant that $Q = !Q'$
2. If S and R transition back to 0 at the same time, Q and Q' begin to oscillate between 1 and 0 because their final values depend on each other (**metastability**)
 - This eventually settles depending on **variation in the circuits**


Memory Element: Latches

 

- A **clock** is a periodic signal that is used to keep time in sequential circuits.
- **Duty Cycle** is the ration of t_w/T_{period}
- We want to keep t_w small so that in the same clock pulse only a single computation is performed.
- We want to keep T_{period} sufficient so that there is enough time for the next input to be computed.

Memory Element: T Latch

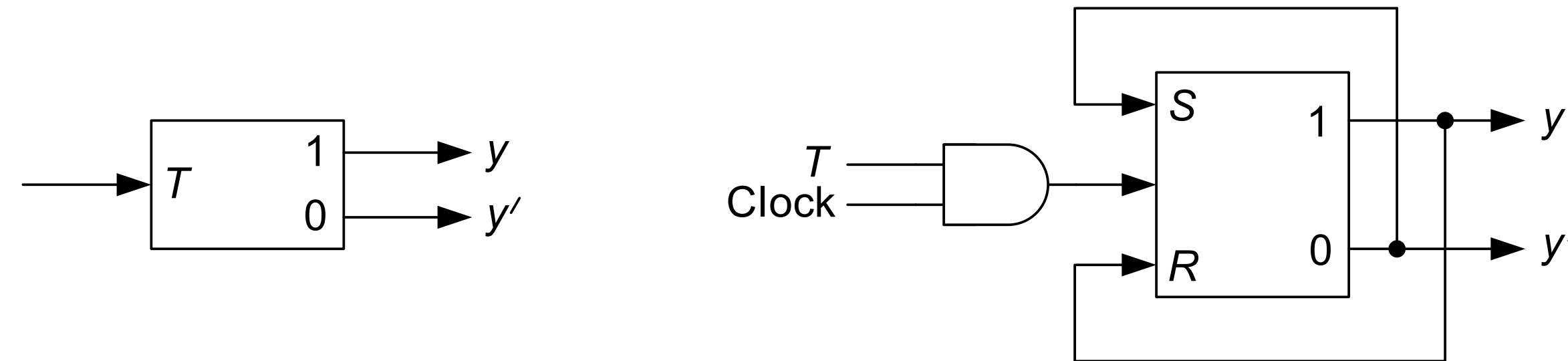Value 1 applied to its input triggers the latch to change state



(a) Block diagram.

(b) Deriving the T latch from the clocked SR latch.

Excitations requirements:

<i>Circuit change</i>		<i>Required value T</i>
<i>From:</i>	<i>To:</i>	
0	0	0
0	1	1
1	0	1
1	1	0

“Q” is basically “y”

Characteristic Table

T Flip-Flop		
T	Q(t + 1)	
0	Q(t)	No change
1	Q'(t)	Complement


$$\begin{aligned}
 y(t+1) &= Ty'(t) + T'y(t) \\
 &= T \oplus y(t)
 \end{aligned}$$

Memory Element: JK Latch

Unlike the *SR* latch, $J = K = 1$ is permitted: when it occurs, the latch acts like a trigger and switches to the complement state



(a) Block diagram.

 

(b) Constructing the JK latch from the clocked SR latch.

Excitation requirements:

Circuit change		Required value	
From:	To:	<i>J</i>	<i>K</i>
0	0	0	–
0	1	1	–
1	0	–	1
1	1	–	0

“Q” is basically “y”

Can you write the characteristic equation?

Characteristic Table


<i>JK</i> Flip-Flop			
<i>J</i>	<i>K</i>	<i>Q</i> (<i>t</i> + 1)	
0	0	<i>Q</i> (<i>t</i>)	No change
0	1	0	Reset
1	0	1	Set
1	1	<i>Q</i> '(<i>t</i>)	Complement

$$y(t + 1) = Jy(t)' + K'y(t)$$


D Latch — The Latch of Your Life

The next state of the D latch is equal to its present excitation:
 $y(t+1) = D(t)$

<i>D</i> Flip-Flop		
<i>D</i>	$Q(t + 1)$	
0	0	Reset
1	1	Set

 

(a) Block diagram.

 

(b) Transforming the JK latch to the D latch.

Excitation Table

Q(t)	Q(t+1)	D
0	0	0
0	1	1
1	0	0
1	1	1

How is Your Clock?

Clocked latch: changes state only in synchronization with the clock pulse and no more than once during each occurrence of the clock pulse

Duration of clock pulse: determined by circuit delays and signal propagation time through the latches


- Must be long enough to allow latch to change state, and
- Short enough so that the latch will not change state twice due to the same excitation

Excitation of a *JK* latch within a sequential circuit:


- Length of the clock pulse must allow the latch to generate the y 's
- But should not be present when the values of the y 's have propagated through the combinational circuit

How fast/slow should be the clock really?

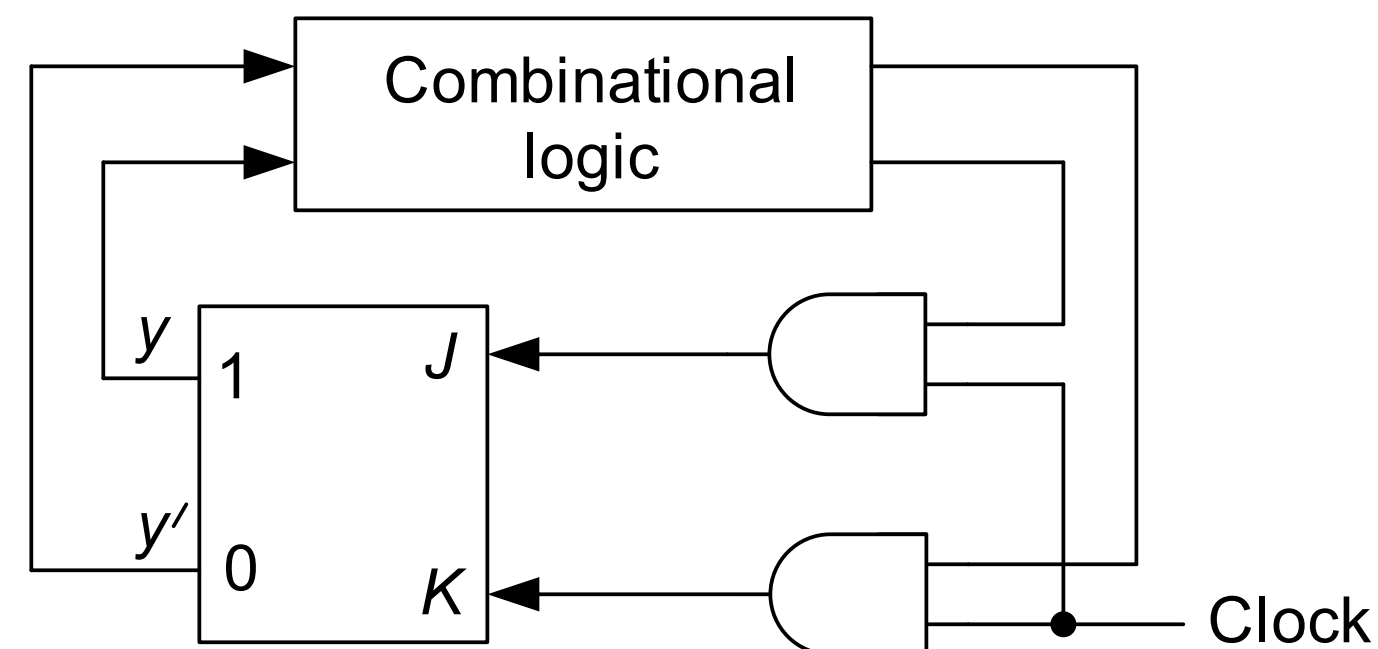
But when does the flip-flop changes its state???



All in One

 

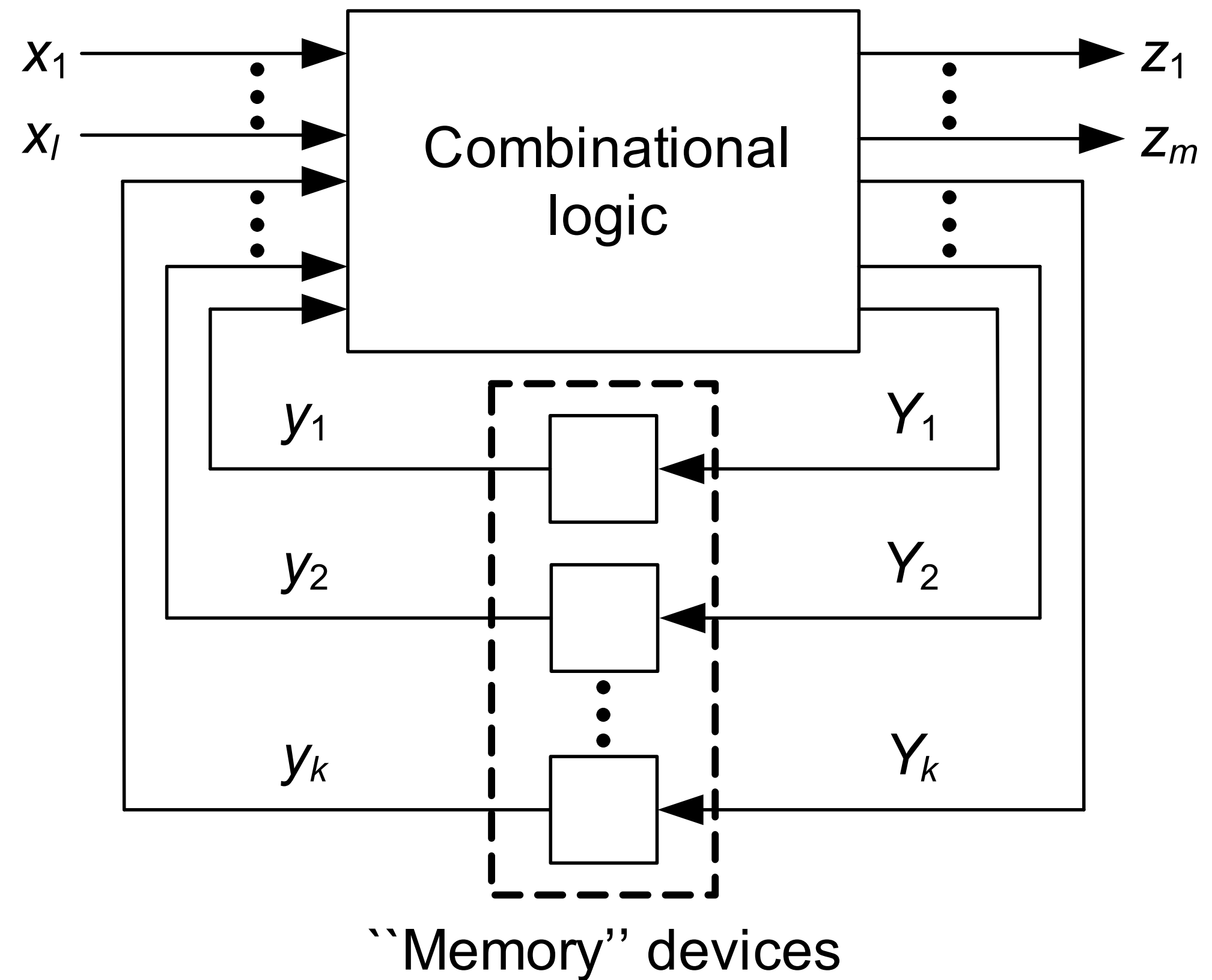D Flip-flop (edge-triggered)
(positive edge triggering)



Delay to make sure all is well


- **Setup time**, t_{su} , is the time period prior to the clock becoming active (edge or level) during which the flip-flop inputs must remain stable.
- **Hold time**, t_h , is the time after the clock becomes inactive during which the flip-flop inputs must remain stable.
- Setup time and hold time define a *window of time during which the flip-flop inputs cannot change* – quiescent interval.

More Delay


- **Propagation delay**, t_{pHL} and t_{pLH} , has the same meaning as in combinational circuit – beware propagation delays usually will not be equal for all input to output pairs. There can be two propagation delays: t_{C-Q} (*clock*→Q delay) and t_{D-Q} (*data*→Q delay).
- For a level or pulse triggered latch:
 - Data input should remain stable till the clock becomes inactive.
 - Clock should remain active till the input change is propagated to Q output. That is, active period of the clock,

$$t_w > \max \{t_{pLH}, t_{pHL}\}$$

The Triggering Dilemma

 

Master Slave Flip-Flop

 


Negative edge triggered flipflop

At a given time, only one latch is alive (either master or slave)


Master Slave Flip-Flop

Master-slave flip-flop: a type of synchronous memory element that eliminates the timing problems by isolating its inputs from its outputs

Master-slave *SR* flip-flop:

 

 Master-slave *JK* flip-flop: since master-slave *SR* flip-flop suffers from the problem that both its inputs cannot be 1, it can be converted to a *JK* flip-flop




Edge Triggered Flip-Flop

Positive (negative) edge-triggered D flip-flop: stores the value at the D input when the clock makes a 0 \rightarrow 1 (1 \rightarrow 0) transition



- Any change at the D input after the clock has made a transition does not have any effect on the value stored in the flip-flop

A negative edge-triggered D flip-flop:

- When the clock is high, the output of the bottommost (topmost) NOR gate is at D' (D), whereas the S - R inputs of the output latch are at 0, causing it to hold previous value
- When the clock goes low, the value from the bottommost (topmost) NOR gate gets transferred as D (D') to the S (R) input of the output latch
 - Thus, output latch stores the value of D
- If there is a change in the value of the D input after the clock has made its transition, the bottommost NOR gate attains value 0
 - However, this cannot change the SR inputs of the output latch

 

Registers: Your Main Sequential Element

 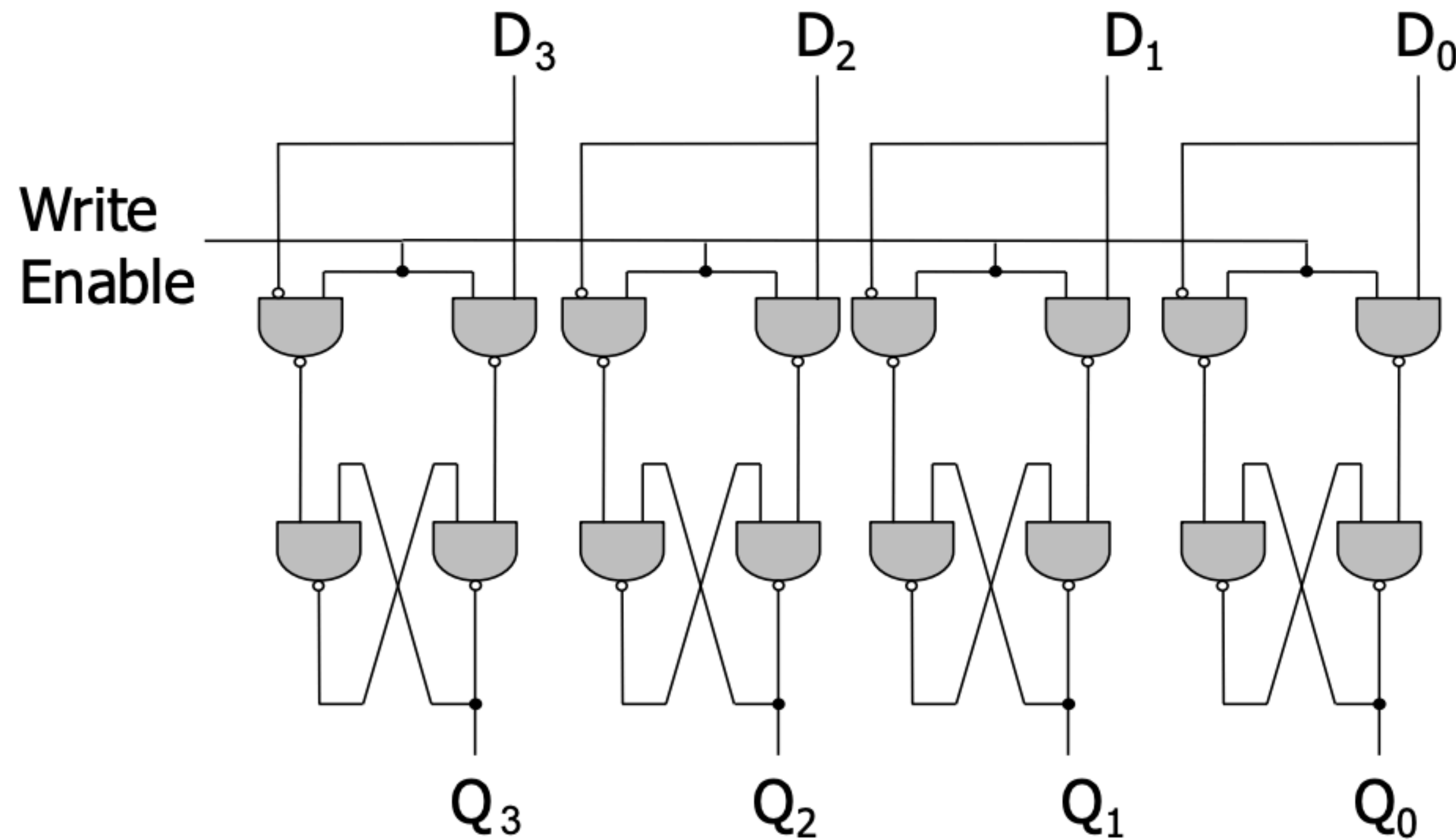

- Used to store data
- Basically an **array of D-flip-flops**
- You can **load data**, reset it to zero, and **shift it to left and right**


Sequential Circuits and Finite State Machines

Sequential circuit: its outputs a function of external inputs as well as stored information (aka. State)

Finite-state machine (FSM): abstract model to describe the synchronous sequential machines. It has finite memory.


Serial binary adder example: You are given a 1-bit adder. But you have to add n-bit numbers

 - First, decide what to remember??
- Then decide how many bits to remember??




$$\begin{array}{rccccc} & t_5 & t_4 & t_3 & t_2 & t_1 & & \\ & 0 & 1 & 1 & 0 & 0 & = & X_1 \\ + & 0 & 1 & 1 & 1 & 0 & = & X_2 \\ \hline & 1 & 1 & 0 & 1 & 0 & = & Z \end{array}$$

 Sequential Circuits and Finite State Machines




Sequential Circuits and Finite State Machines

 - Let **A** denote the state of the adder at t_i if the carry 0 is generated at t_{i-1}
- Let **B** denote the state of the adder at t_i if the carry 1 is generated at t_{i-1}



 
$$\begin{array}{rcccccc}
 & t_5 & t_4 & t_3 & t_2 & t_1 & \\
 & 0 & 1 & 1 & 0 & 0 & = X_1 \\
 + & 0 & 1 & 1 & 1 & 0 & = X_2 \\
 \hline
 & 1 & 1 & 0 & 1 & 0 & = Z
 \end{array}$$




Sequential Circuits and Finite State Machines

 - Let **A** denote the state of the adder at t_i if the carry 0 is generated at t_{i-1}
- Let **B** denote the state of the adder at t_i if the carry 1 is generated at t_{i-1}



PS	NS, z			
	$x_1x_2 = 00$	01	11	10
A	$A, 0$	$A, 1$	$B, 0$	$A, 1$
B	$A, 1$	$B, 0$	$B, 1$	$B, 0$
 
$$\begin{array}{r}
 \begin{array}{cccccc}
 & t_5 & t_4 & t_3 & t_2 & t_1 \\
 & 0 & 1 & 1 & 0 & 0 \\
 & = & X_1 \\
 + & 0 & 1 & 1 & 1 & 0 \\
 & = & X_2 \\
 \hline
 & 1 & 1 & 0 & 1 & 0 \\
 & = & Z
 \end{array}
 \end{array}$$




Sequential Circuits and Finite State Machines

FSMs: whose past histories can affect their future behavior in only a finite number of ways

- **Serial adder:** its response to the signals at time t is only a function of these signals and the value of the carry at $t-1$
 - Thus, its input histories can be grouped into just two classes: those resulting in a 1 carry and those resulting in a 0 carry at t
- **Thus, every finite-state machine contains a finite number of memory devices:** which store the information regarding the past input history

 Sequential Circuits and Finite State Machines



Input variables: $\{x_1, x_2, \dots, x_l\}$

Input configuration, symbol, pattern or vector: ordered l -tuple of 0's and 1's

Input alphabet: set of $p = 2^l$ distinct input patterns

- Thus, input alphabet $I = \{I_1, I_2, \dots, I_p\}$
- Example: for two variables x_1 and x_2
 - $I = \{00, 01, 10, 11\}$

Output variables: $\{z_1, z_2, \dots, z_m\}$

Output configuration, symbol, pattern or vector: ordered m -tuple of 0's and 1's

Output alphabet: set of $q = 2^m$ distinct output patterns

- Thus, output alphabet $O = \{O_1, O_2, \dots, O_q\}$

Synthesis of Synchronous Sequential Circuits

Main steps:


1. From a word description of the problem, form a **state diagram** or **table**
2. Select a **state assignment** and determine the type of memory elements
3. Derive **transition** and **output** tables
4. Derive an **excitation table** and obtain **excitation** and **output functions**
from their respective tables
5. Draw a **circuit diagram**

Synthesis of Synchronous Sequential Circuits

One-input/one-output sequence detector: produces output value 1 every time sequence 0101 is detected, else 0

- Example: 010101 -> 000101

State diagram and state table:

 


<i>PS</i>	<i>NS, z</i>	
	<i>x</i> = 0	<i>x</i> = 1
<i>A</i>	<i>B</i> , 0	<i>A</i> , 0
<i>B</i>	<i>B</i> , 0	<i>C</i> , 0
<i>C</i>	<i>D</i> , 0	<i>A</i> , 0
<i>D</i>	<i>B</i> , 0	<i>C</i> , 1

Synthesis of Synchronous Sequential Circuits

One-input/one-output sequence detector: produces output value 1 every time sequence 0101 is detected, else 0

- Example: 010101 -> 000101

State diagram and state table:

 

<i>PS</i>	<i>NS, z</i>	
	<i>x</i> = 0	<i>x</i> = 1
<i>A</i>	<i>B</i> , 0	<i>A</i> , 0
<i>B</i>	<i>B</i> , 0	<i>C</i> , 0
<i>C</i>	<i>D</i> , 0	<i>A</i> , 0
<i>D</i>	<i>B</i> , 0	<i>C</i> , 1


Transition and output tables:

<i>y</i> ₁ <i>y</i> ₂	<i>Y</i> ₁ <i>Y</i> ₂		<i>z</i>	
	<i>x</i> = 0	<i>x</i> = 1	<i>x</i> = 0	<i>x</i> = 1
<i>A</i> → 00	01	00	0	0
<i>B</i> → 01	01	11	0	0
<i>C</i> → 11	10	00	0	0
<i>D</i> → 10	01	11	0	1


D Latch — The Latch of Your Life

The next state of the D latch is equal to its present excitation:
 $y(t+1) = D(t)$

D Flip-Flop		
D	$Q(t + 1)$	
0	0	Reset
1	1	Set

 

(a) Block diagram.

 

(b) Transforming the JK latch to the D latch.

Excitation Table

$Q(t)$	$Q(t+1)$	D
0	0	0
0	1	1
1	0	0
1	1	1

Synthesis of Synchronous Sequential Circuits

Excitation Table

Q(t)	Q(t+1)	D
0	0	0
0	1	1
1	0	0
1	1	1

- Let us use DFF as our state elements
- We need 2 DFFs as our state is 2 bit
- Now how to set the inputs of the DFFs??

y_1y_2	Y_1Y_2		z	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
$A \rightarrow 00$	01	00	0	0
$B \rightarrow 01$	01	11	0	0
$C \rightarrow 11$	10	00	0	0
$D \rightarrow 10$	01	11	0	1

Synthesis of Synchronous Sequential Circuits

Excitation Table

Q(t)	Q(t+1)	D
0	0	0
0	1	1
1	0	0
1	1	1


- Let us use DFF as our state elements
- We need 2 DFFs as our state is 2 bit
- Now how to set the inputs of the DFFs??

y_1y_2	Y_1Y_2		z		D(Y1)		D(Y2)	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$	$x = 0$	$x = 1$	$x = 0$	$x = 1$
$A \rightarrow 00$	01	00	0	0	0	0	1	0
$B \rightarrow 01$	01	11	0	0	0	1	1	1
$C \rightarrow 11$	10	00	0	0	1	0	0	0
$D \rightarrow 10$	01	11	0	1	0	1	1	1

Synthesis of Synchronous Sequential Circuits

Excitation Table

Q(t)	Q(t+1)	D
0	0	0
0	1	1
1	0	0
1	1	1


 


y_1y_2	Y_1Y_2		z		D(Y1)		D(Y2)	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$	$x = 0$	$x = 1$	$x = 0$	$x = 1$
$A \rightarrow 00$	01	00	0	0	0	0	1	0
$B \rightarrow 01$	01	11	0	0	0	1	1	1
$C \rightarrow 11$	10	00	0	0	1	0	0	0
$D \rightarrow 10$	01	11	0	1	0	1	1	1

Synthesis of Synchronous Sequential Circuits

Excitation Table

Q(t)	Q(t+1)	D
0	0	0
0	1	1
1	0	0
1	1	1

  

y_1y_2	Y_1Y_2		z		D(Y1)		D(Y2)	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$	$x = 0$	$x = 1$	$x = 0$	$x = 1$
$A \rightarrow$	00	00	0	0	0	0	1	0
$B \rightarrow$	01	11	0	0	0	1	1	1
$C \rightarrow$	11	00	0	0	1	0	0	0
$D \rightarrow$	10	11	0	1	0	1	1	1

Synthesis of Synchronous Sequential Circuits

Excitation Table

Q(t)	Q(t+1)	D
0	0	0
0	1	1
1	0	0
1	1	1

$y_1y_2 \backslash x$	x	
	0	1
00		
01		
11		
10		1

(a) z map.

$y_1y_2 \backslash x$	x	
	0	1
00		
01		1
11	1	
10		1

(b) Y_1 map.

$y_1y_2 \backslash x$	x	
	0	1
00	1	
01	1	1
11		
10	1	1

(c) Y_2 map.

y_1y_2	Y_1Y_2		z	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
$A \rightarrow$	00	00	0	0
$B \rightarrow$	01	11	0	0
$C \rightarrow$	11	00	0	0
$D \rightarrow$	10	11	0	1

D(Y1)		D(Y2)	
x = 0	x = 1	x=0	x=1
0	0	1	0
0	1	1	1
1	0	0	0
0	1	1	1

Synthesis of Synchronous Sequential Circuits

Excitation Table

Q(t)	Q(t+1)	D
0	0	0
0	1	1
1	0	0
1	1	1

$y_1y_2 \backslash x$	x	
	0	1
00		
01		
11		
10		1

(a) z map.

$y_1y_2 \backslash x$	x	
	0	1
00		
01		1
11	1	
10		1

(b) Y_1 map.

$y_1y_2 \backslash x$	x	
	0	1
00	1	
01	1	1
11		
10	1	1

(c) Y_2 map.

$$z = xy_1y_2'$$
$$Y_1 = x'y_1y_2 + xy_1'y_2 + xy_1y_2'$$
$$Y_2 = y_1y_2' + x'y_1' + y_1'y_2$$

y_1y_2	Y_1Y_2		z		$D(Y_1)$		$D(Y_2)$	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$	$x = 0$	$x = 1$	$x = 0$	$x = 1$
$A \rightarrow$	00	00	0	0	0	0	1	0
$B \rightarrow$	01	11	0	0	0	1	1	1
$C \rightarrow$	11	00	0	0	1	0	0	0
$D \rightarrow$	10	11	0	1	0	1	1	1


Synthesis of Synchronous Sequential Circuits

Excitation Table


Q(t)	Q(t+1)	D
0	0	0
0	1	1
1	0	0
1	1	1

y_1y_2	Y_1Y_2		z	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
$A \rightarrow 00$	01	00	0	0
$B \rightarrow 01$	01	11	0	0
$C \rightarrow 11$	10	00	0	0
$D \rightarrow 10$	01	11	0	1


D(Y1)		D(Y2)	
x = 0	x = 1	x=0	x=1
0	0	1	0
0	1	1	1
1	0	0	0
0	1	1	1

 

(a) z map.

 


(b) Y_1 map.

 

(c) Y_2 map.

$$\begin{aligned} z &= xy_1y_2', \\ Y_1 &= x'y_1y_2 + xy_1'y_2 + xy_1y_2', \\ Y_2 &= y_1y_2' + x'y_1' + y_1'y_2 \end{aligned}$$

Logic Diagram

 

Synthesis of Synchronous Sequential Circuits

Another state assignment:


y_1y_2	Y_1Y_2		z	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
$A \rightarrow 00$	01	00	0	0
$B \rightarrow 01$	01	10	0	0
$C \rightarrow 10$	11	00	0	0
$D \rightarrow 11$	01	10	0	1

$$z = xy_1y_2$$
$$Y_1 = x'y_1y_2' + xy_2$$
$$Y_2 = x'$$

Binary Counter

One-input/one-output modulo-8 binary counter: produces output value 1 for every eighth input 1 value

State diagram and state table:

 

<i>PS</i>	<i>NS</i>		<i>Output</i>	
	<i>x</i> = 0	<i>x</i> = 1	<i>x</i> = 0	<i>x</i> = 1
<i>S</i> ₀	<i>S</i> ₀	<i>S</i> ₁	0	0
<i>S</i> ₁	<i>S</i> ₁	<i>S</i> ₂	0	0
<i>S</i> ₂	<i>S</i> ₂	<i>S</i> ₃	0	0
<i>S</i> ₃	<i>S</i> ₃	<i>S</i> ₄	0	0
<i>S</i> ₄	<i>S</i> ₄	<i>S</i> ₅	0	0
<i>S</i> ₅	<i>S</i> ₅	<i>S</i> ₆	0	0
<i>S</i> ₆	<i>S</i> ₆	<i>S</i> ₇	0	0
<i>S</i> ₇	<i>S</i> ₇	<i>S</i> ₀	0	1


Binary Counter

Transition and output tables:

PS $y_3y_2y_1$	NS		z		$T_3T_2T_1$	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$	$x = 0$	$x = 1$
000	000	001	0	0	000	001
001	001	010	0	0	000	011
010	010	011	0	0	000	001
011	011	100	0	0	000	111
100	100	101	0	0	000	001
101	101	110	0	0	000	011
110	110	111	0	0	000	001
111	111	000	0	1	000	111

Excitation table for T

<i>Circuit change</i>		<i>Required value T</i>
<i>From:</i>	<i>To:</i>	
0	0	0
0	1	1
1	0	1
1	1	0

 


Binary Counter with SR Flip Flops

Transition and output tables:

<i>PS</i> <i>y₃y₂y₁</i>	<i>NS</i>		<i>z</i>		<i>x</i> = 0			<i>x</i> = 1		
	<i>x</i> = 0	<i>x</i> = 1	<i>x</i> = 0	<i>x</i> = 1	<i>S₃R₃</i>	<i>S₂R₂</i>	<i>S₁R₁</i>	<i>S₃R₃</i>	<i>S₂R₂</i>	<i>S₁R₁</i>
000	000	001	0	0	0–	0–	0–	0–	0–	10
001	001	010	0	0	0–	0–	–0	0–	10	01
010	010	011	0	0	0–	–0	0–	0–	–0	10
011	011	100	0	0	0–	–0	–0	10	01	01
100	100	101	0	0	–0	0–	0–	–0	0–	10
101	101	110	0	0	–0	0–	–0	–0	10	01
110	110	111	0	0	–0	–0	0–	–0	–0	10
111	111	000	0	1	–0	–0	–0	01	01	01

Excitation table for *SR* flip-flops and logic diagram:

<i>Circuit change</i>		<i>Required value</i>	
<i>From:</i>	<i>To:</i>	<i>S</i>	<i>R</i>
0	0	0	–
0	1	1	0
1	0	0	1
1	1	–	0

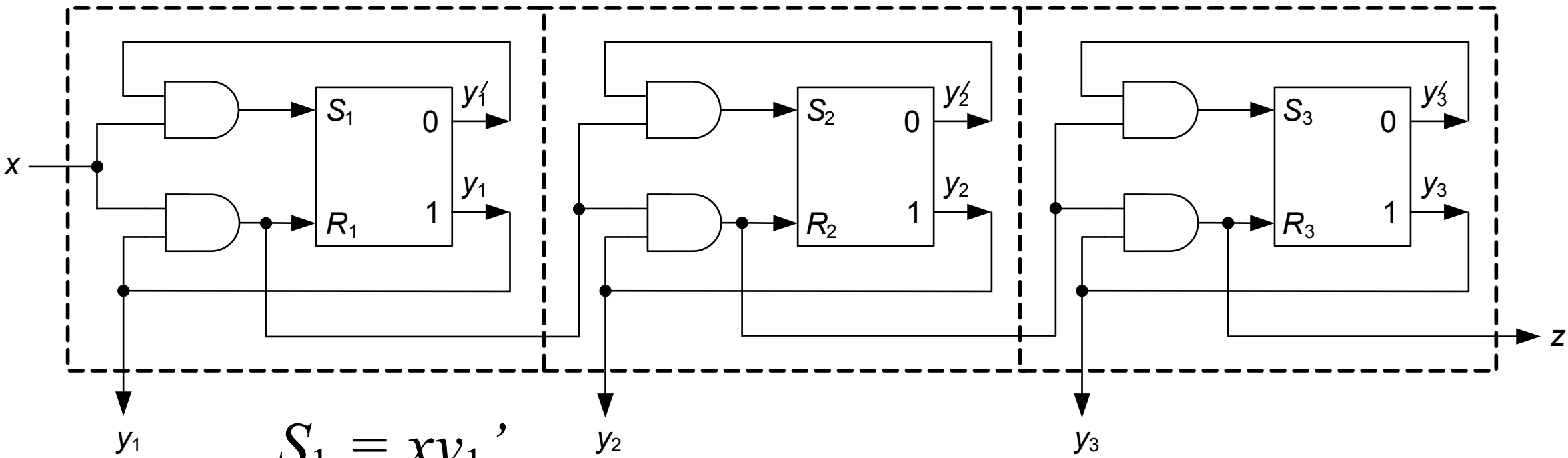

$$\begin{aligned} S_1 &= xy_1' \\ R_1 &= xy_1 \\ S_2 &= xy_1y_2' \\ R_2 &= xy_1y_2 \\ S_3 &= xy_1y_2y_3' \\ R_3 &= z = xy_1y_2y_3 \end{aligned}$$

But...Life is Beautiful End of the day...

```
always @(posedge clk) begin
    if (rst)
        count <= 3'b000;    // Reset to 0
    else if (count == 3'b111) // If 7, wrap back to 0
        count <= 3'b000;
    else
        count <= count + 1'b1; // Increment
end
```